

**SSR DEGREE & PG COLLEGE (AUTONOMOUS) NIZAMABAD**

**M.SC. PHYSICS**

**SEM – II INTERNAL – II**

**ELECTRONICS - 2**

**QUESTION BANK**

**I. Multiple Choice**

1. A counter is a

- a) Memory device
- b) Sequential circuit
- c) Combinational circuit
- d) Amplifier

Answer: b) Sequential circuit

2. Which counter counts in binary sequence?

- a) Ring counter
- b) Binary counter
- c) Johnson counter
- d) Shift counter

Answer: b) Binary counter

3. A mod-10 counter is also called

- a) Binary counter
- b) Decade counter
- c) Ring counter
- d) Up counter

Answer: b) Decade counter

4. Ripple counter is also known as

- a) Synchronous counter
- b) Asynchronous counter
- c) Ring counter
- d) Down counter

Answer: b) Asynchronous counter

5. In a synchronous counter, all flip-flops are triggered by

- a) Different clocks
- b) External pulses
- c) Same clock pulse
- d) Output pulse

Answer: c) Same clock pulse

6. MOD number of a counter indicates

- a) Number of flip-flops
- b) Counting speed
- c) Number of states
- d) Frequency

Answer: c) Number of states

7. A 4-bit binary counter has how many states?

- a) 4
- b) 8
- c) 16
- d) 32

Answer: c) 16

8. Ring counter uses

- a) Capacitors
- b) Shift registers
- c) Resistors
- d) Diodes

Answer: b) Shift registers

9. Which counter can count upward and downward?

- a) Ring counter
- b) Johnson counter
- c) Up-down counter
- d) Ripple counter

Answer: c) Up-down counter

10. Counter circuits are mainly used for

- a) Amplification

- b) Timing and counting
- c) Rectification
- d) Oscillation

Answer: b) Timing and counting

11. ADC converts

- a) Digital signal to analog signal
- b) Analog signal to digital signal
- c) AC to DC
- d) DC to AC

Answer: b) Analog signal to digital signal

12. The output of ADC is in

- a) Decimal form
- b) Binary form
- c) Analog form
- d) Sinusoidal form

Answer: b) Binary form

13. Which ADC is the fastest?

- a) Counter type ADC
- b) Dual slope ADC
- c) Flash ADC
- d) Successive approximation ADC

Answer: c) Flash ADC

14. Resolution of ADC depends on

- a) Input voltage
- b) Number of bits
- c) Frequency
- d) Power supply

Answer: b) Number of bits

15. Quantization error occurs in

- a) DAC
- b) Oscillator

c) ADC

d) Amplifier

Answer: c) ADC

16. Successive approximation ADC uses

a) Comparator

b) Counter

c) Shift register

d) Encoder

Answer: a) Comparator

17. Higher resolution ADC gives

a) Lower accuracy

b) Better accuracy

c) Lower speed

d) Higher noise

18. Answer: b) Better accuracy

ADC is commonly used in

a) Digital voltmeters

b) Loudspeakers

c) Rectifiers

d) Motors

Answer: a) Digital voltmeters

19. The full form of ADC is

a) Automatic Digital Converter

b) Analog to Digital Converter

c) Analog Data Controller

d) Automatic Data Converter

Answer: b) Analog to Digital Converter

20. In ADC, sampling is required for

a) Continuous signals

b) Analog signals

c) Digital signals

d) AC signals only

Answer: b) Analog signals

## II. Fill in the blanks

1. A counter is a \_\_\_\_ circuit.

Answer: sequential

2. A counter that counts from 0 to 9 is called a \_\_\_\_ counter.

Answer: decade

3. In a synchronous counter, all flip-flops receive the \_\_\_\_ pulse simultaneously.

Answer: clock

4. Ripple counter is also called an \_\_\_\_ counter.

Answer: asynchronous

5. A 4-bit binary counter has \_\_\_\_ possible states.

Answer: 16

6. Counters are mainly used for \_\_\_\_ and timing operations.

Answer: counting

7. Ring counter is constructed using \_\_\_\_ registers.

Answer: shift

8. An up-down counter can count in \_\_\_\_ directions.

Answer: both

9. MOD of a counter indicates the number of \_\_\_\_.

Answer: states

10. Flip-flops are the basic building blocks of \_\_\_\_.

Answer: counters

11. A counter is a \_\_\_\_ circuit.

Answer: sequential

12. A counter that counts from 0 to 9 is called a \_\_\_\_ counter.

Answer: decade

13. In a synchronous counter, all flip-flops receive the \_\_\_\_ pulse simultaneously.

Answer: clock

14. Ripple counter is also called an \_\_\_\_ counter.

Answer: asynchronous

15. A 4-bit binary counter has \_\_\_\_ possible states.

Answer: 16

16. Counters are mainly used for \_\_\_\_ and timing operations.

Answer: counting

17. Ring counter is constructed using \_\_\_\_ registers.

Answer: shift

18. An up-down counter can count in \_\_\_\_ directions.

Answer: both

19. MOD of a counter indicates the number of \_\_\_\_.

Answer: states

20. Flip-flops are the basic building blocks of \_\_\_\_.

Answer: counters

### III. Descriptive Question

1. Draw the block diagram of decade counter
2. Draw the block diagram of R -2R ladder network DAC
3. Explain successive approximation ADC
4. Draw the architecture of 8085 microprocessor
5. Classify instruction set of 8085 microprocessor